



EE DEPARTMENT, IIT BOMBAY

20TH FEB 2025

TUE - 08

MILESTONE - 2

STRUCTURAL HEALTH MONITORING SYSTEM
USING DSPIC33A

TABLE OF CONTENT

01

Review from Milestone 1

02

Overview of project management plan and documentation

03

Progress made against test plan and any deviation from original

04

Block diagram with details

05

Analysis/Calculations/Simulation Results

06

Circuit diagram (schematic) of various circuit boards and wiring diagrams of different systems

07

Details of test plans and Preliminary testing

08

Moving Forward..!

REVIEW OF MILESTONE - 1

- Efficient work distribution of components for better understanding and deeper analysis, schematic making etc.
- Do extensive testing for each components and then use.
- Power amplifier could not amplify to 100Vpp at 150MHz(our operating frequency) hence we need to change it.
- SMPS was not isolated power supply(AC side and DC side should be separated) hence we need to also change it.
- For Pulse C setting we required a Clipping circuit to reject the unwanted forthcoming high voltage signal(basically our sent signal) to burn our ADC

OVERVIEW OF PROJECT PLAN MANAGMENT

- PCB – Plan of Action
 - 1. Component Allocation
 - 2. Reading of Datasheets
 - 3. Simulation and Obtaining Peripheral Values
 - 4. Knowledge Transfer
 - 5. Designed Schematic
- ComSol Simulation – Plan of Action
 - 1. Attachment of PZT Sensor
 - 2. Generation of Hanning Pulse
 - 3. Excitation of PZT in Shear Mode
 - 4. Plotted Results for Ideal Aluminum Plating

OVERVIEW OF PROJECT PLAN MANAGMENT

- Testing Plan of Action:
 - Reading the datasheet for DsPIC and the testing components, and them writing Embedded C code for testing components.
 - Components tested include ADC, DAC, and INA.

DOCUMENTATION

- For the clipping circuit, we initially used operational amplifiers (op-amps) to generate a voltage of less than 2V, as confirmed by our simulation results.
- This voltage level was safer for the ADC.
- However, after consulting with Sheetal Mam, we were advised to simplify the design by using diodes instead.
- Consequently, we created a diode-based clipping circuit, with one diode placed before the instrumentation amplifier (INA) and another placed after it.
- Our simulations confirmed that this setup also worked effectively.


DOCUMENTATION

- Earlier, we were using LM741 to generate the Hanning pulse, which has a very low slew rate of 0.
- After a review, we were advised to use an operational amplifier (op-amp) with a high slew rate of approximately $20 \text{ V}/\mu\text{s}$.
- As a result, we switched to TL072CP, which has a slew rate of $20 \text{ V}/\mu\text{s}$.
- All other PCB-related simulations and COMSOL tasks were successfully completed, which will be covered in the upcoming slides.



BLOCK DIAGRAM

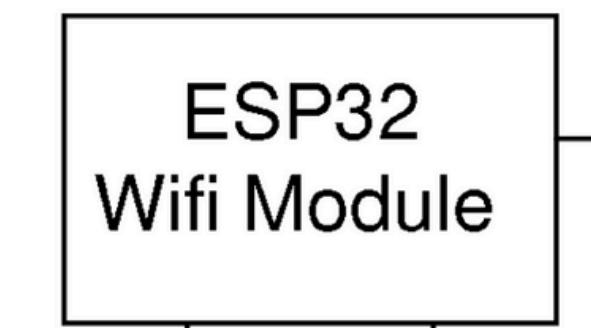
Used to wirelessly receive base model from PC and receive data values from microcontroller via UART.
 $V_{in} = 3.3V$





Digital Hanning
Pulse to Analog
Waveform
 $V_{dd} = 5V$,



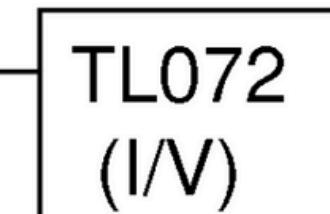Amplification of 4 for
high voltage and high
frequency signal
 $+V_s = +48V, -V_s = -48V$,
 $I_{out} = 15A$



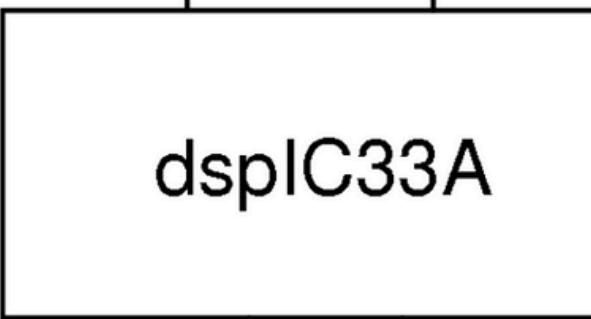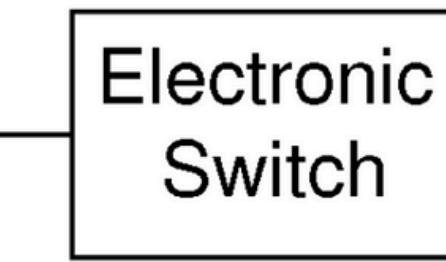High voltage switching for
selecting the PZT for
transmitting
 $I = 3A, V_{dd} = 5V, V_{pp} = -48V$,
 $V_{nn} = 48V, Clk = 5MHz$




Used to store data
 $V_{in} = 2.2V$ to $5.5V$



Amplify voltage from
mV to 1V
 $V_{ss+} = 15V, V_{ss-} = -15V$
 $V_{in} = (\text{in mV}), V_{out} = 1V$



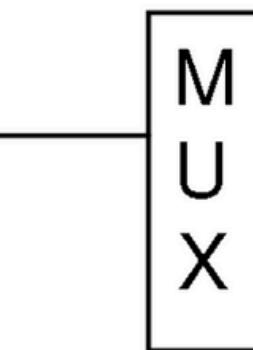
Clip out the of higher
amplitude to bring
down in suitable range
 $V_{in} \text{ range} = 0 \text{ to } 70V$
 $V_{out} = 0 \text{ to } 0.7V$



8 out 1 of one PZT
is multiplexed
 $V_s = +48V$
 $-V_s = -48V$,





WIRING DIAGRAM

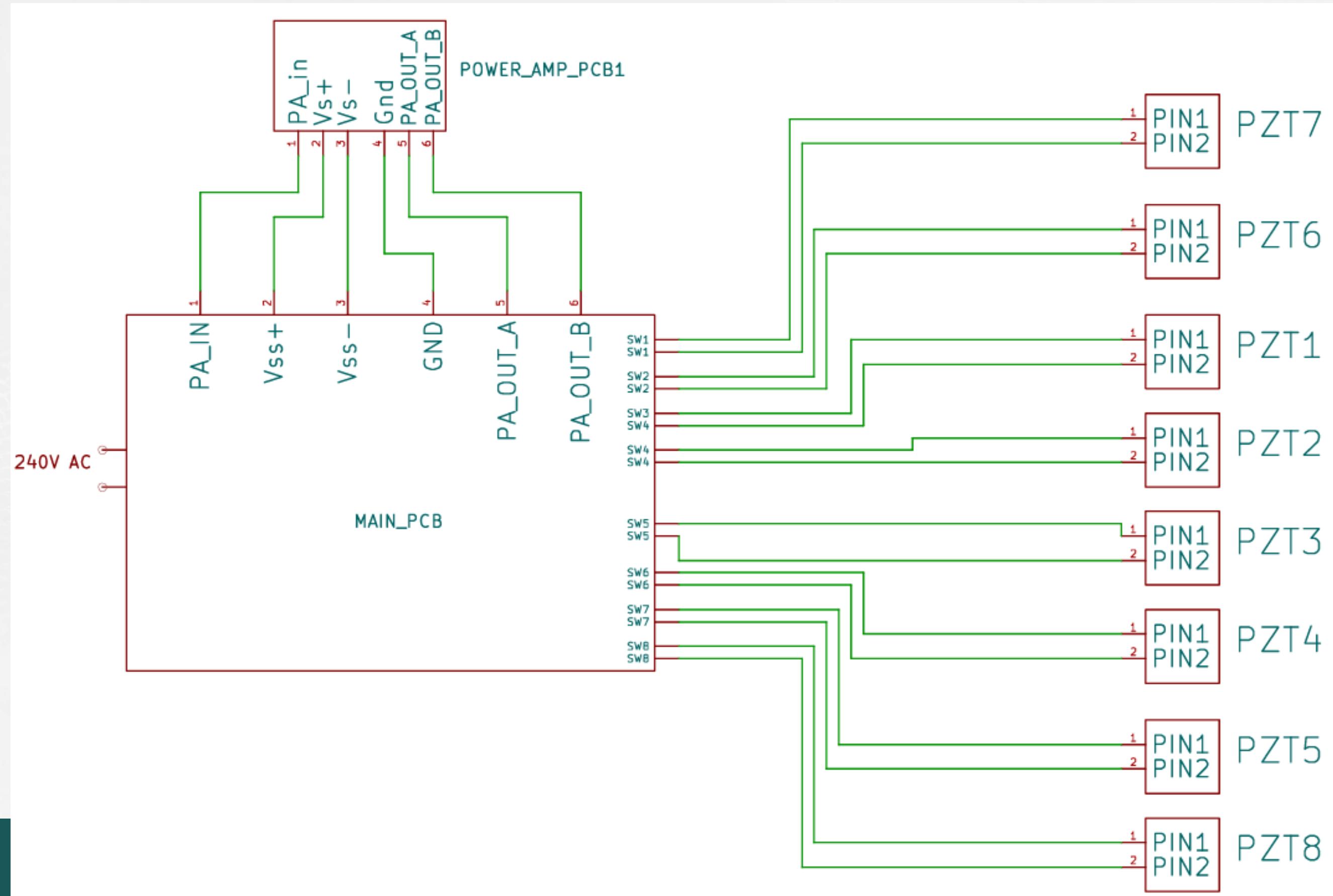

SCHEMATIC MODULES


POWER AMPLIFIER

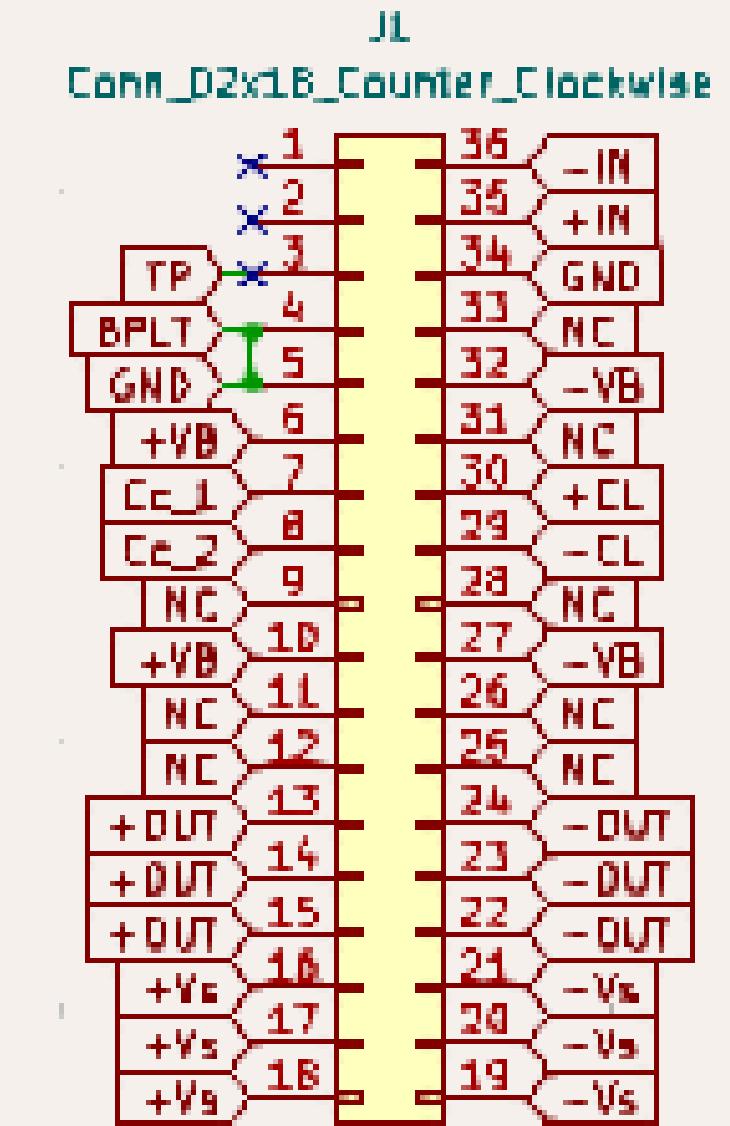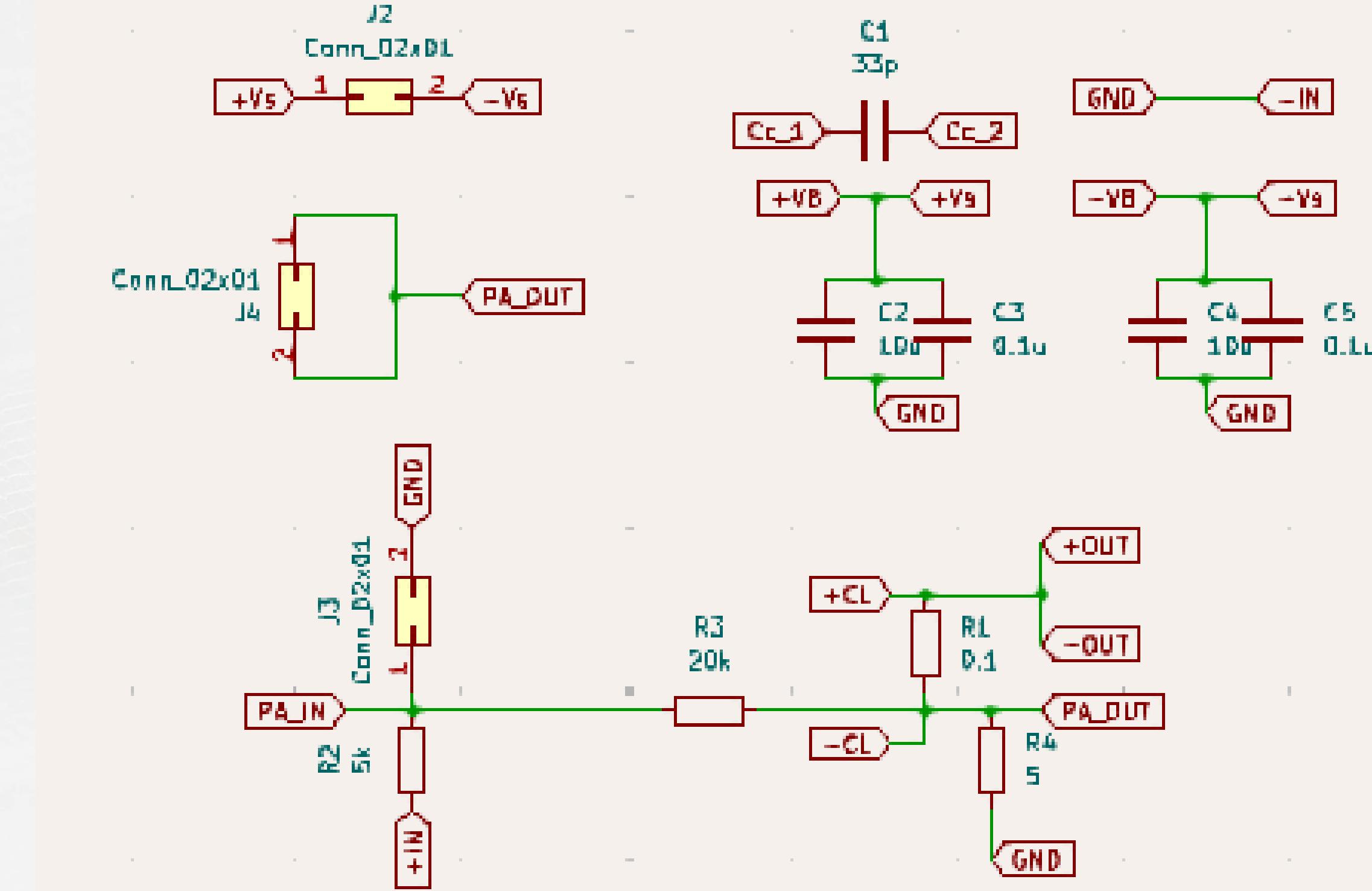


POWER AMPLIFIER

WIFI MODULE


WiFi Module

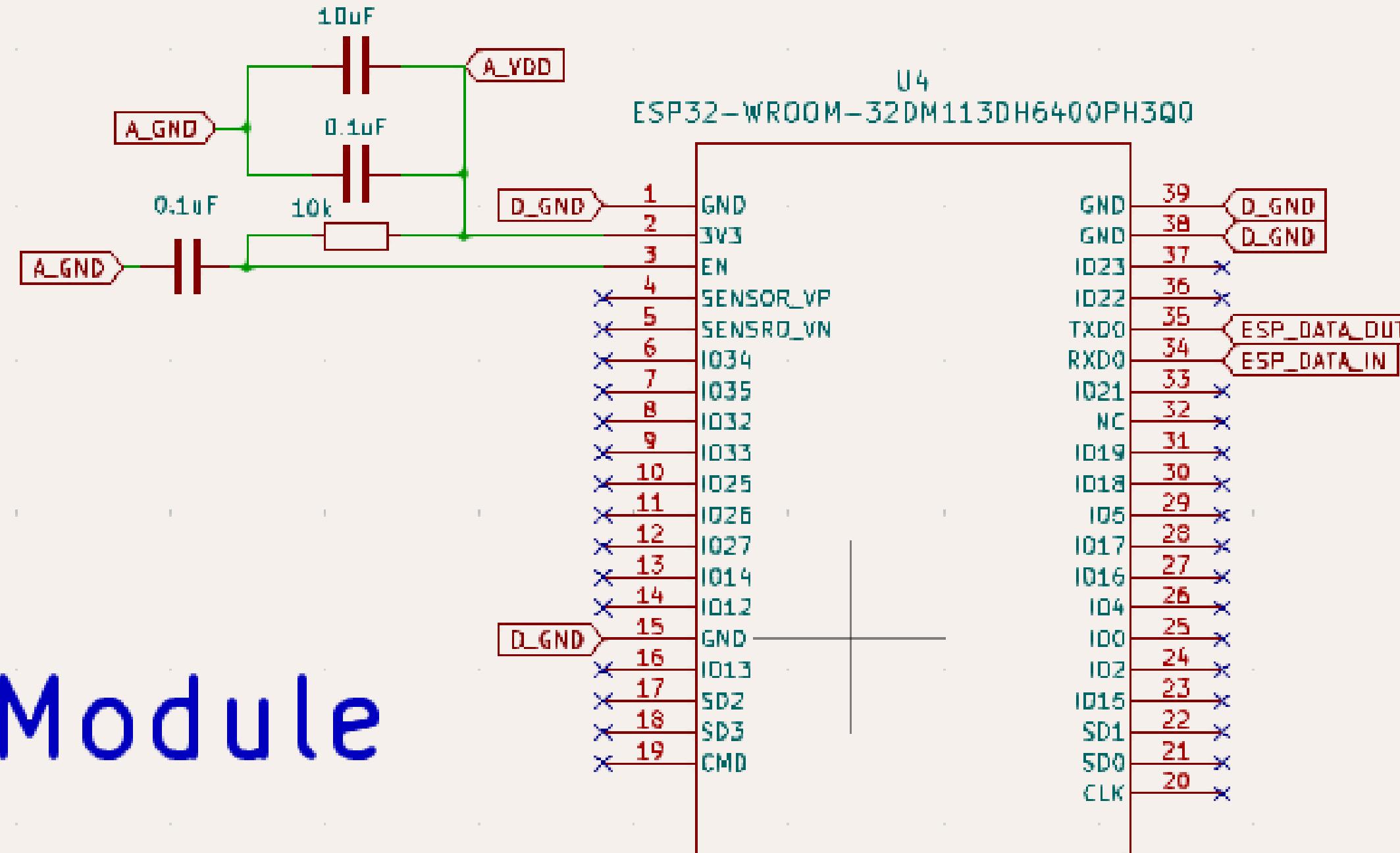

POWER SUPPLY - 1

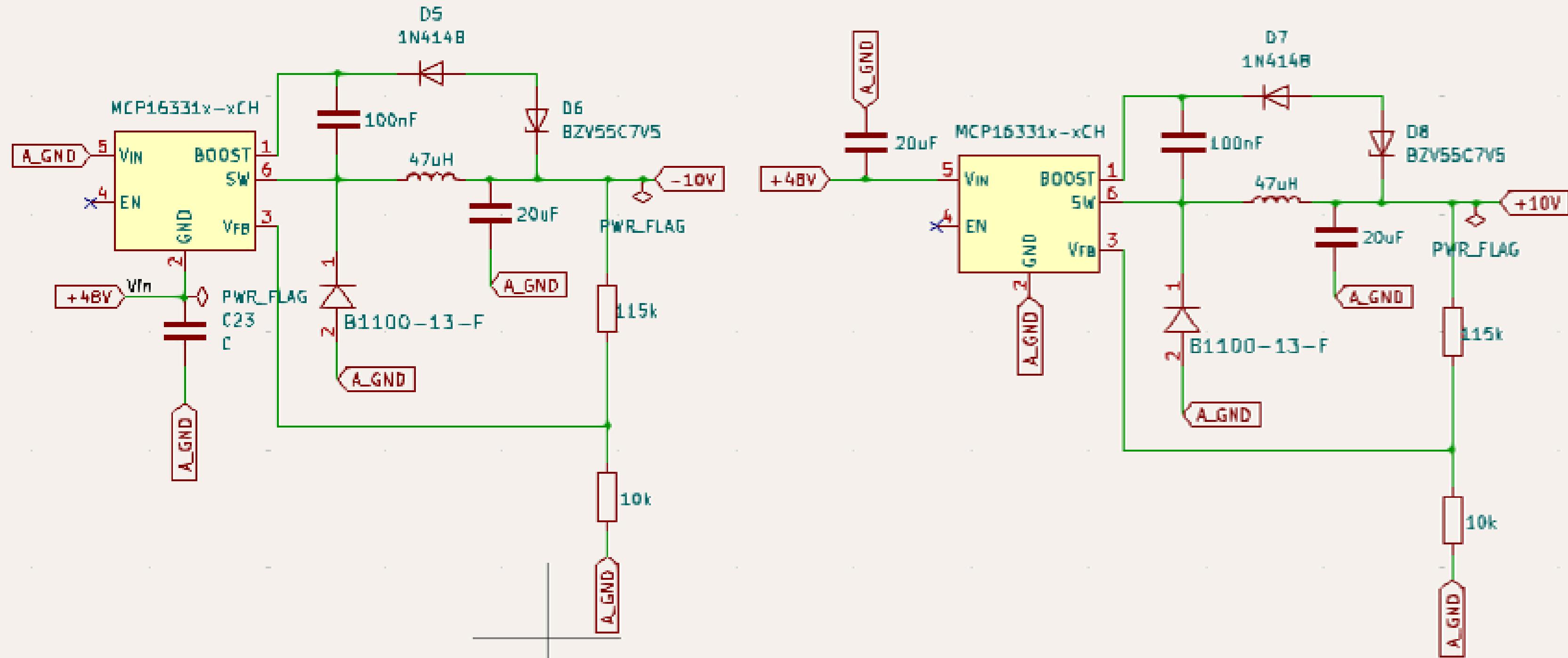


POWER SUPPLY - 2

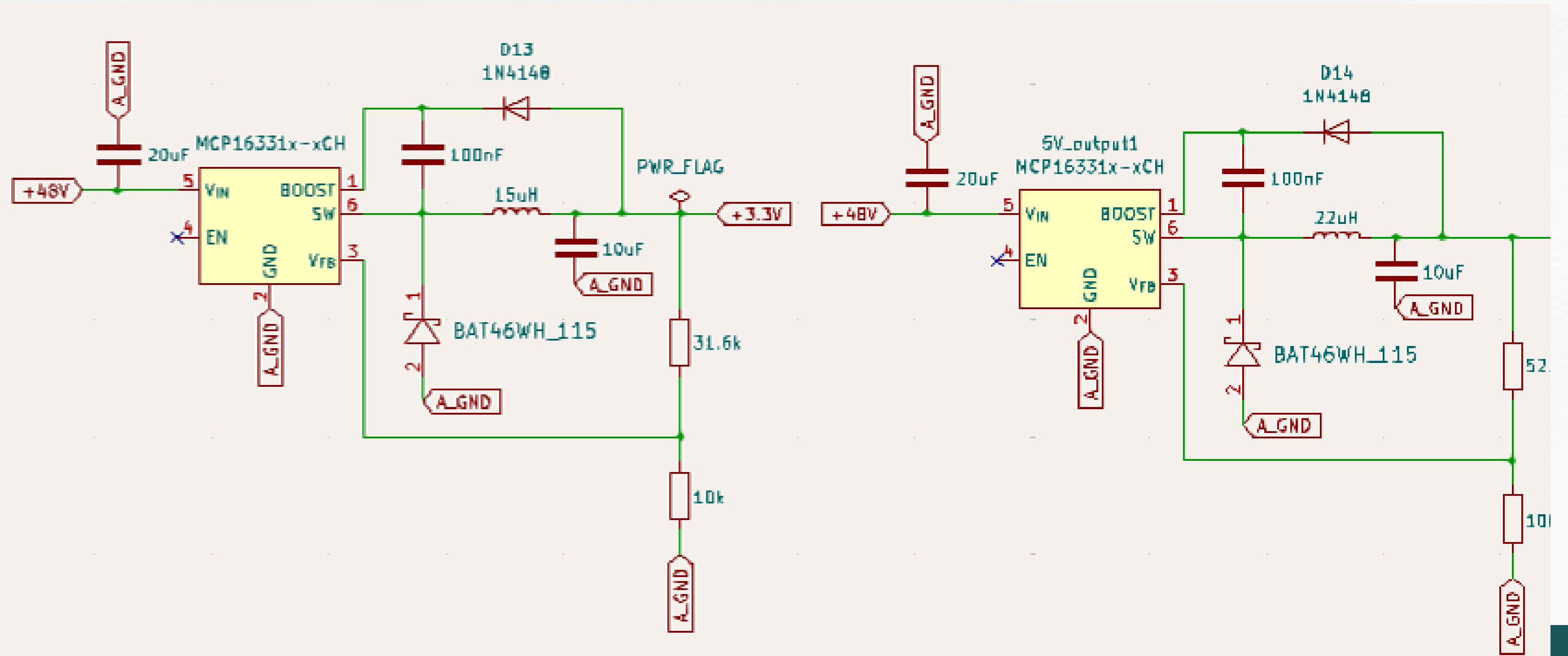


MEMORY (SRAM)

IC1
25LCV04N-I_{ST}

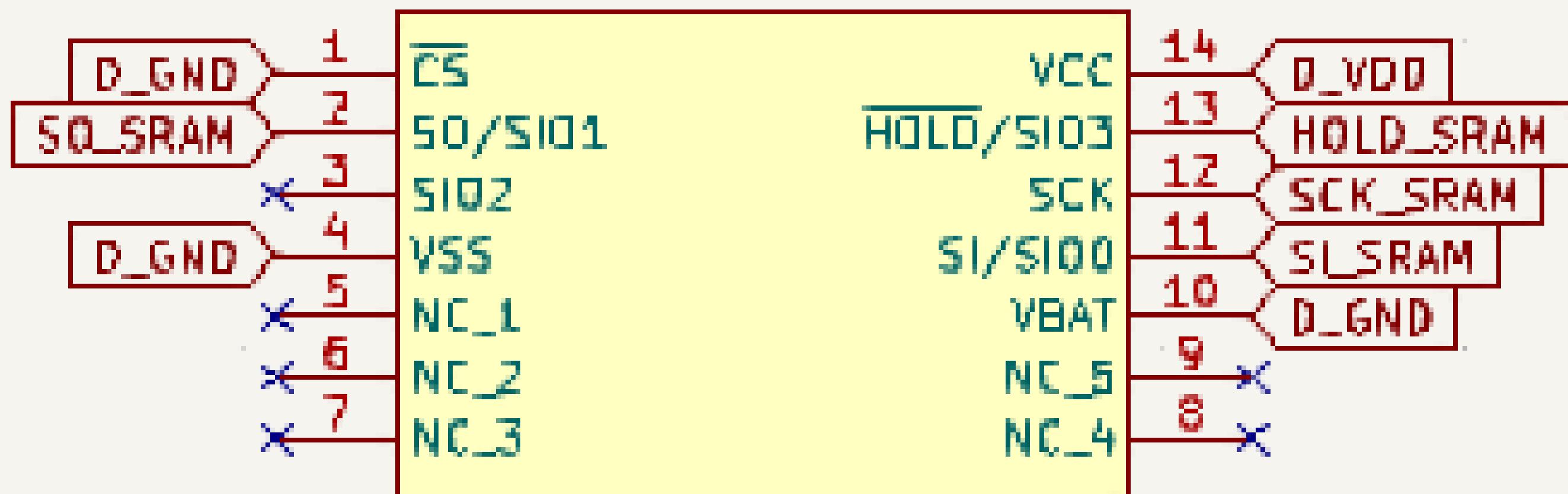


POWER AMPLIFIER SELECT SWITCH

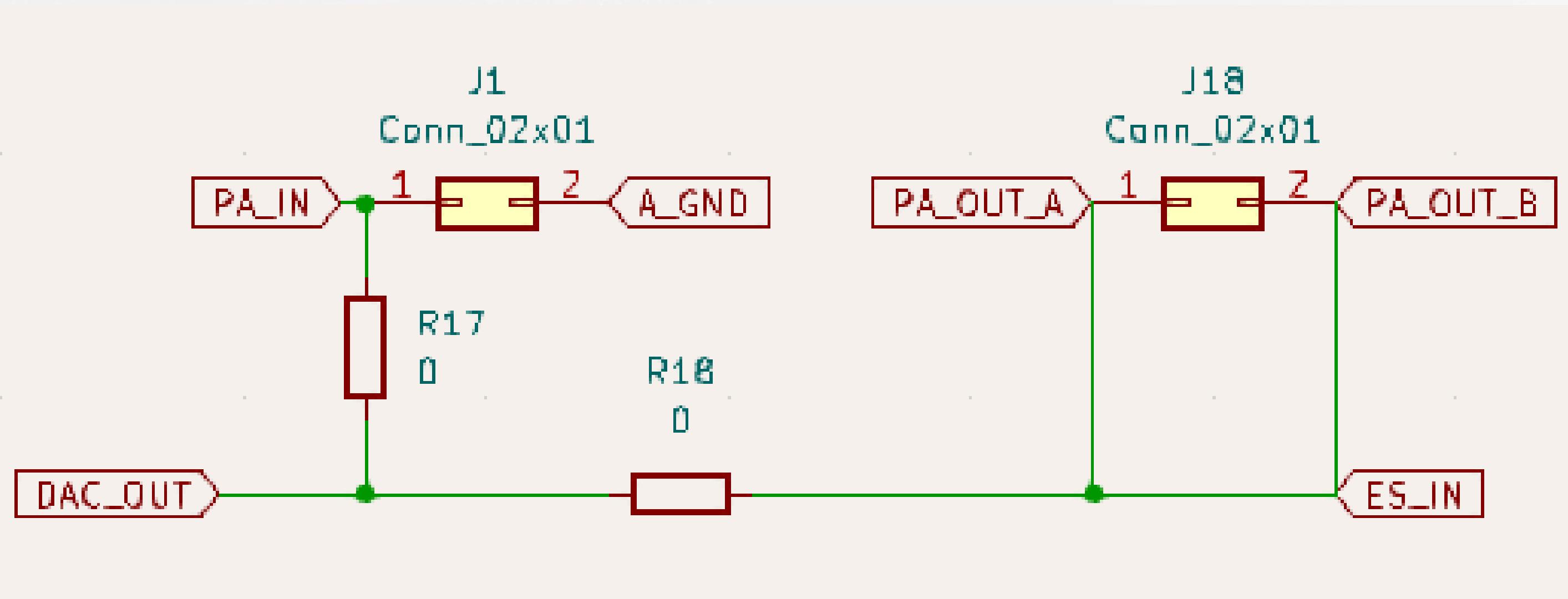


MULTIPLEXER


U6
TMUX8108PWR

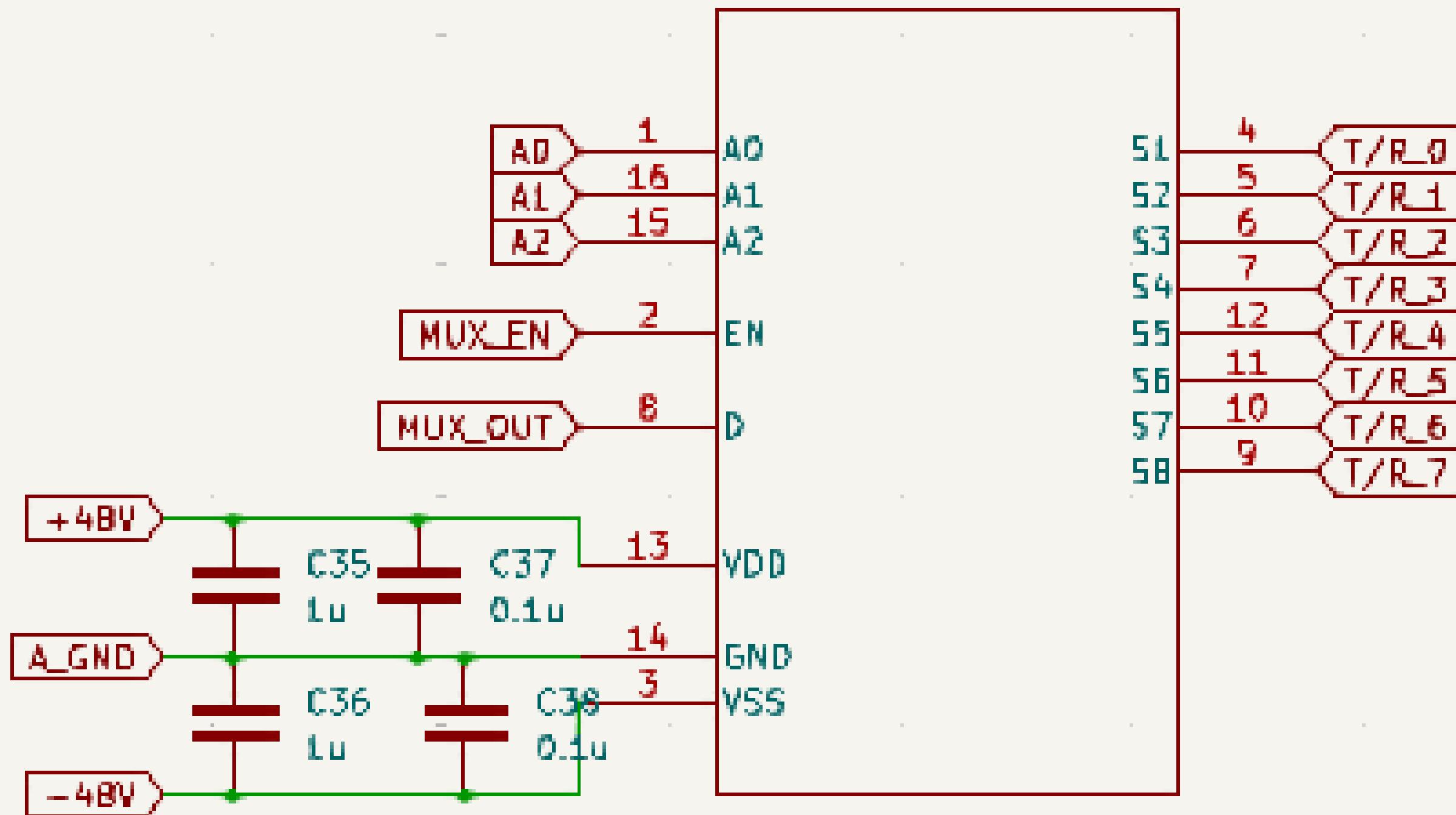

ADC MODULE

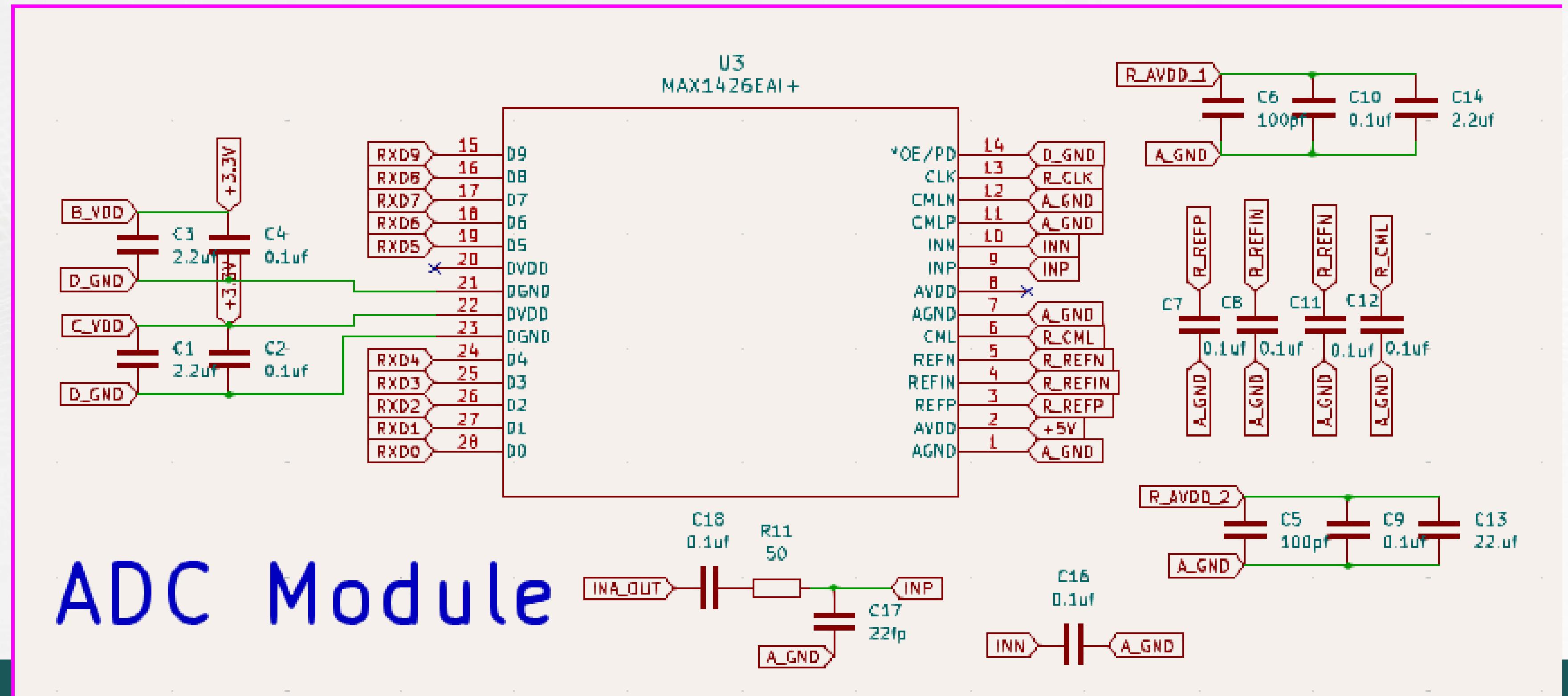


OUTPUT BNC AND SCREW

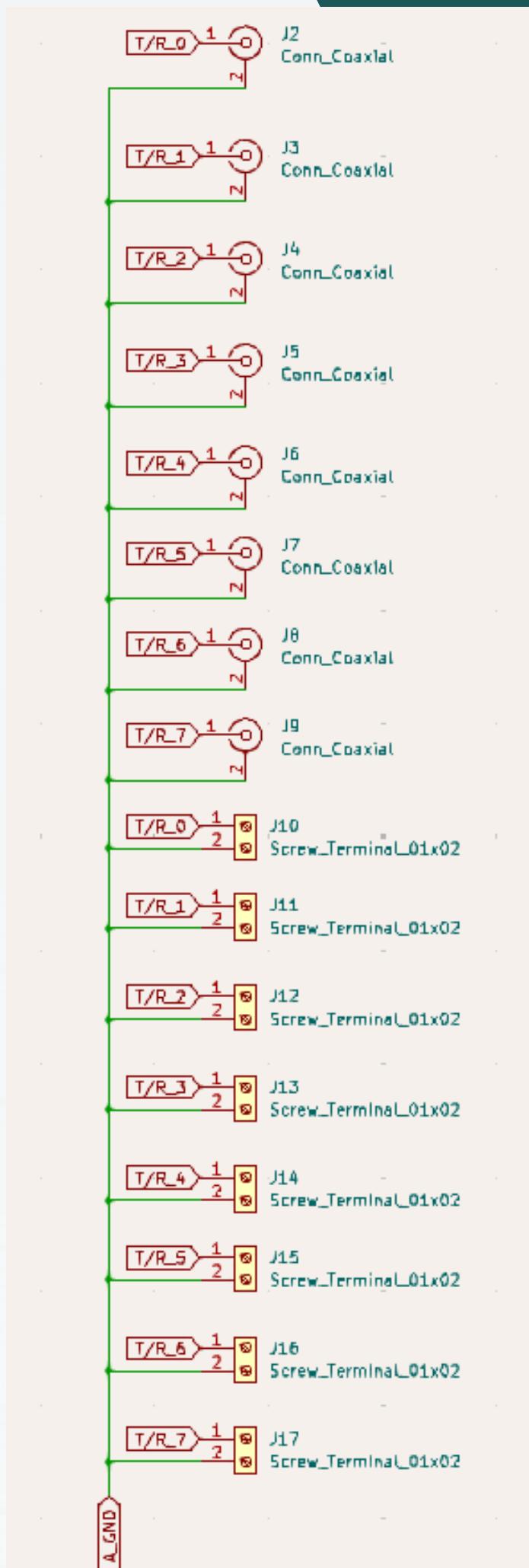



Output

DAC MODULE

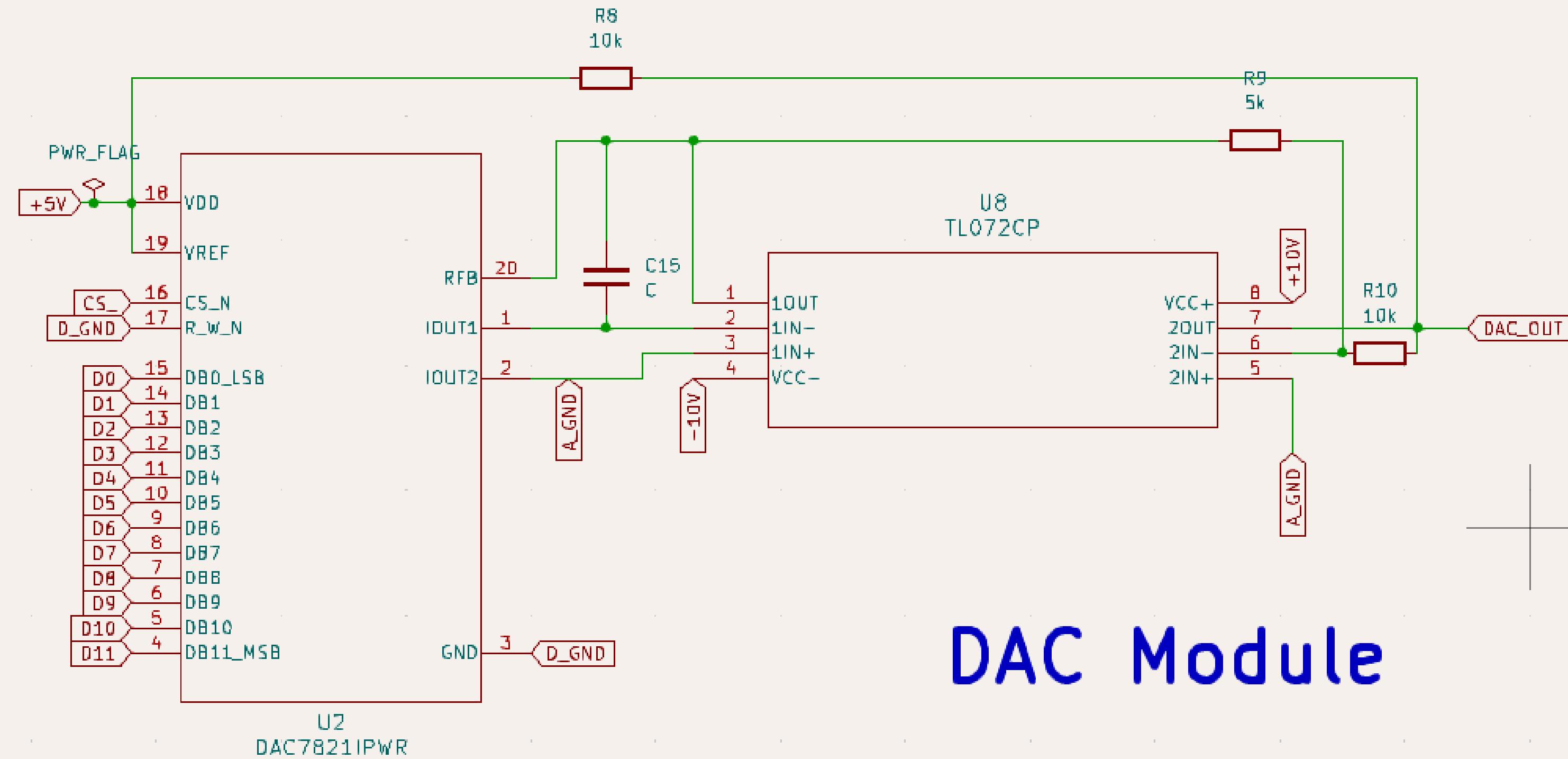


DSPIC33AK128MC106 MICROCONTROLLER

Programming
Interface

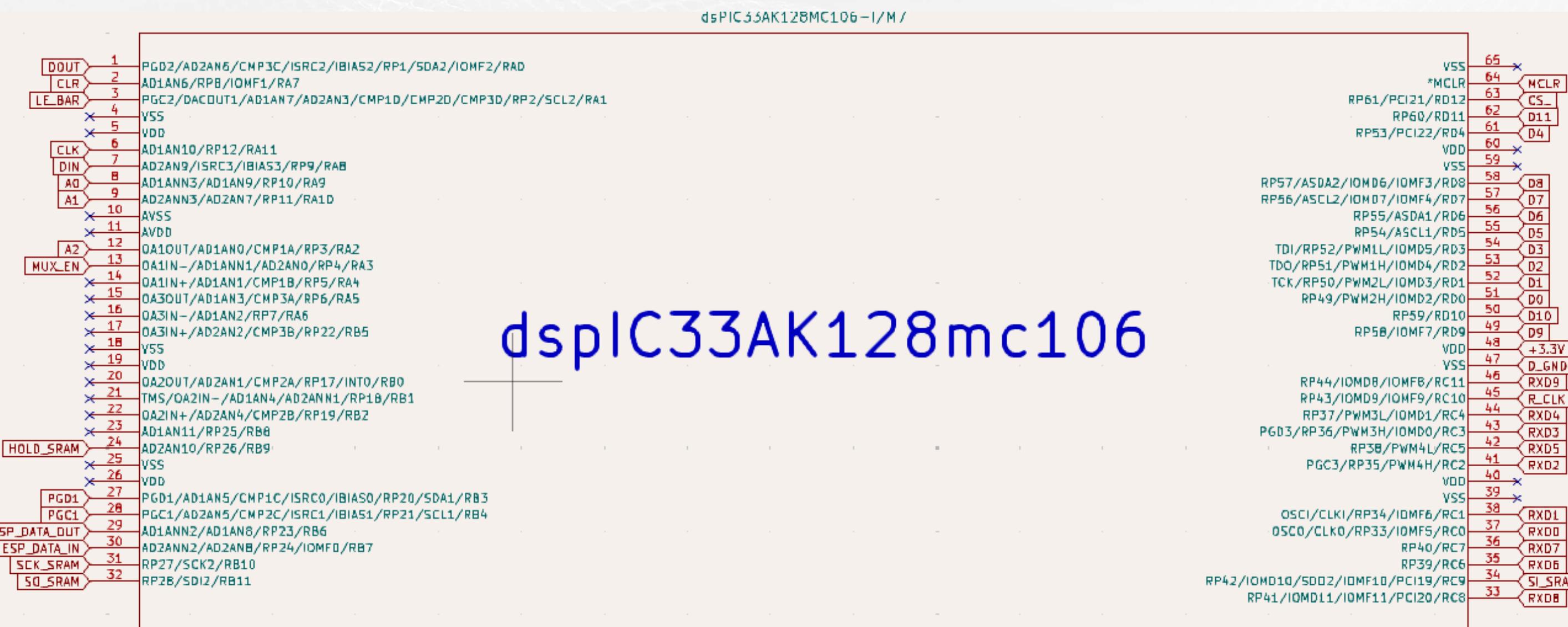
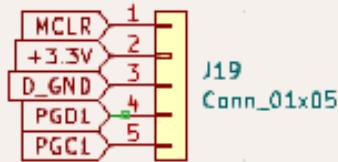


ELECTRONIC SWITCHES

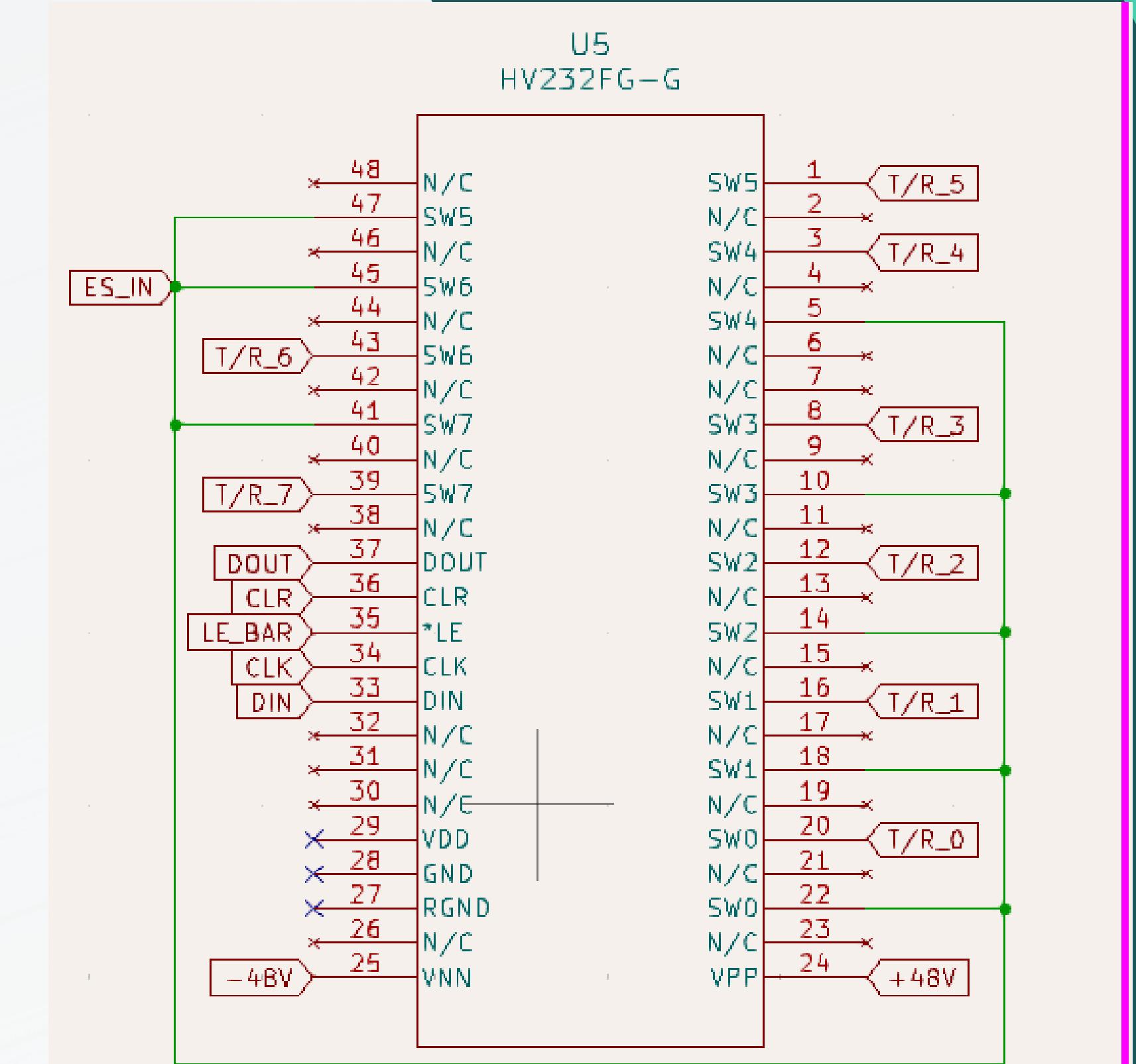


Electronic Switches

CLIPPING CIRCUIT+ INA128

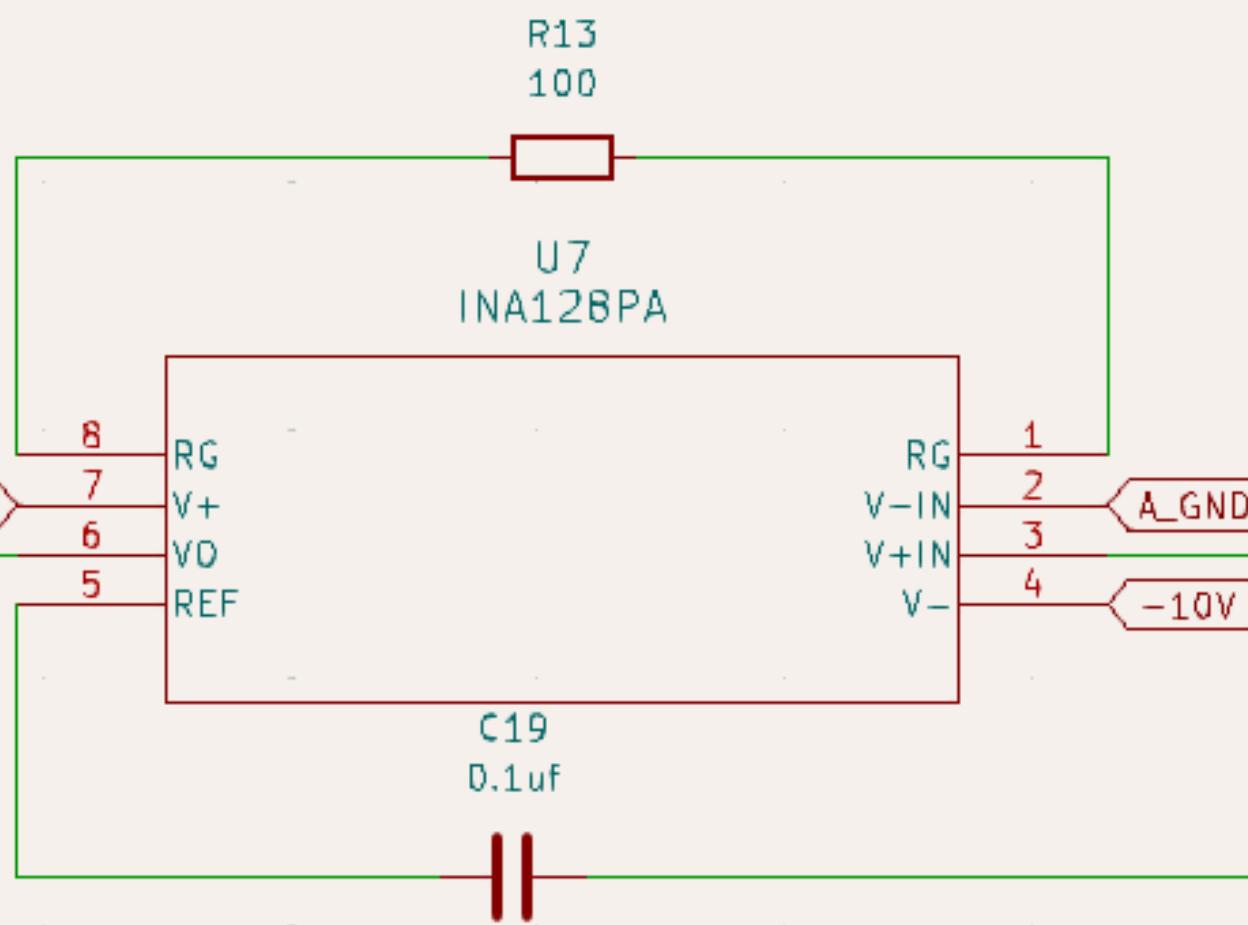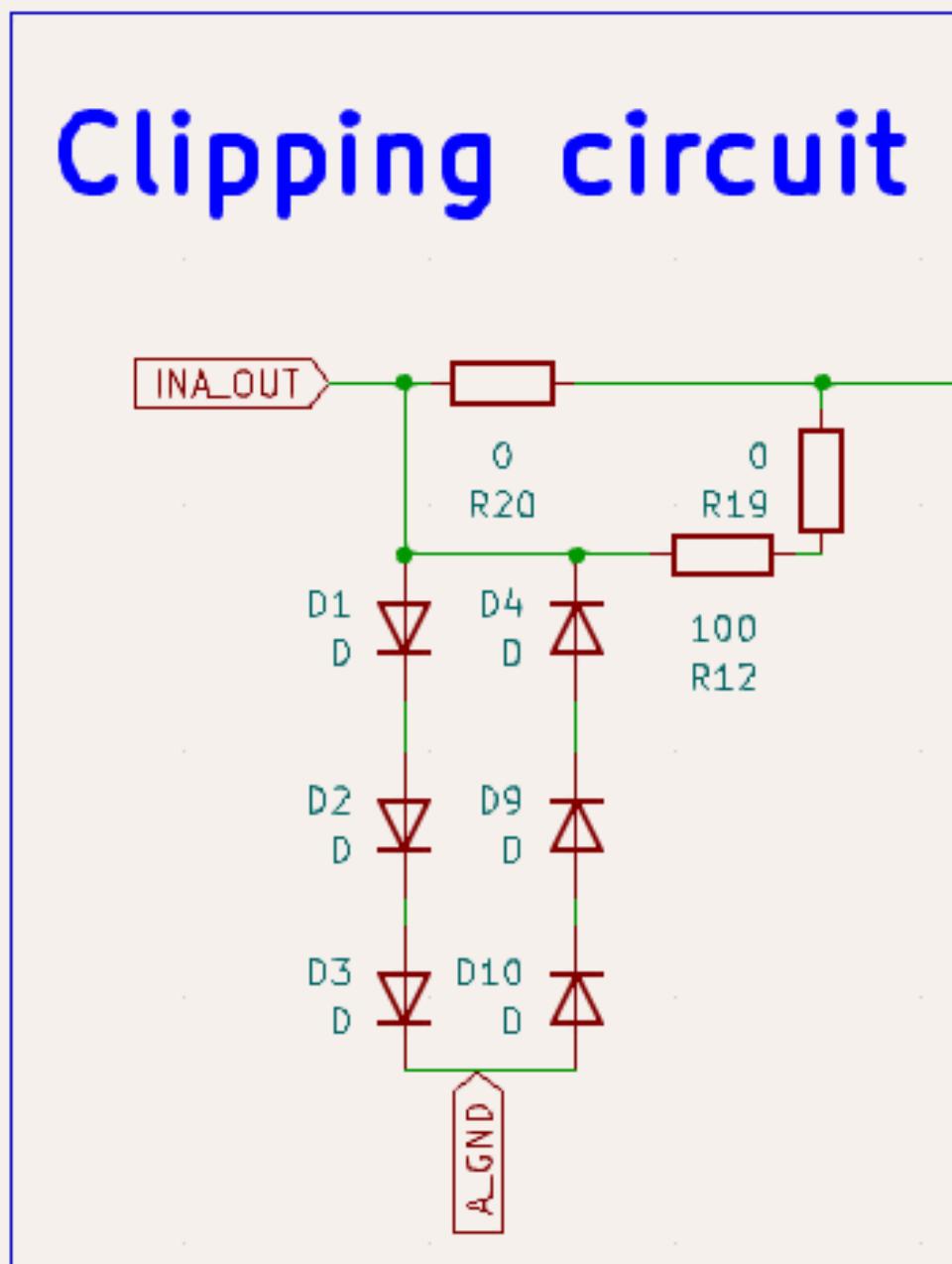


INA 128

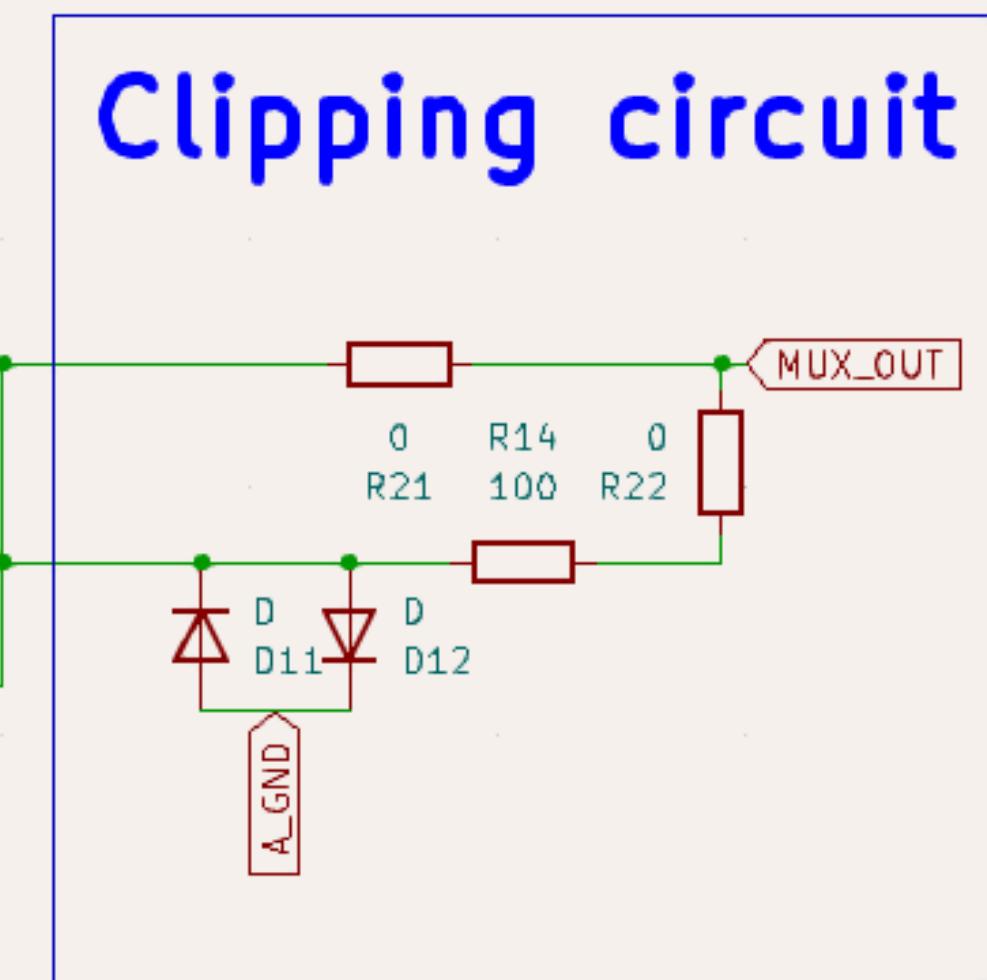


SIMULATIONS RESULTS


INA + CLIPPER CKT

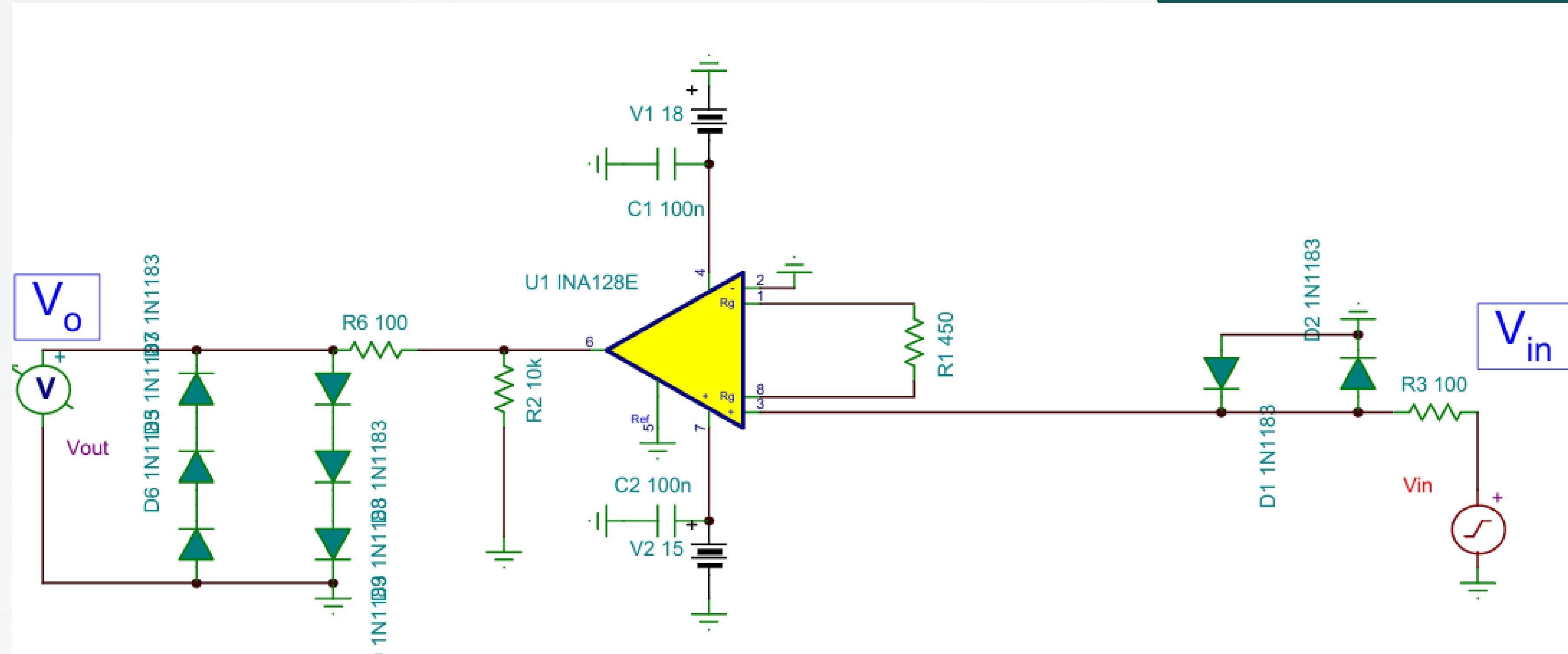


INA + CLIPPER FOR 1MV INPUT

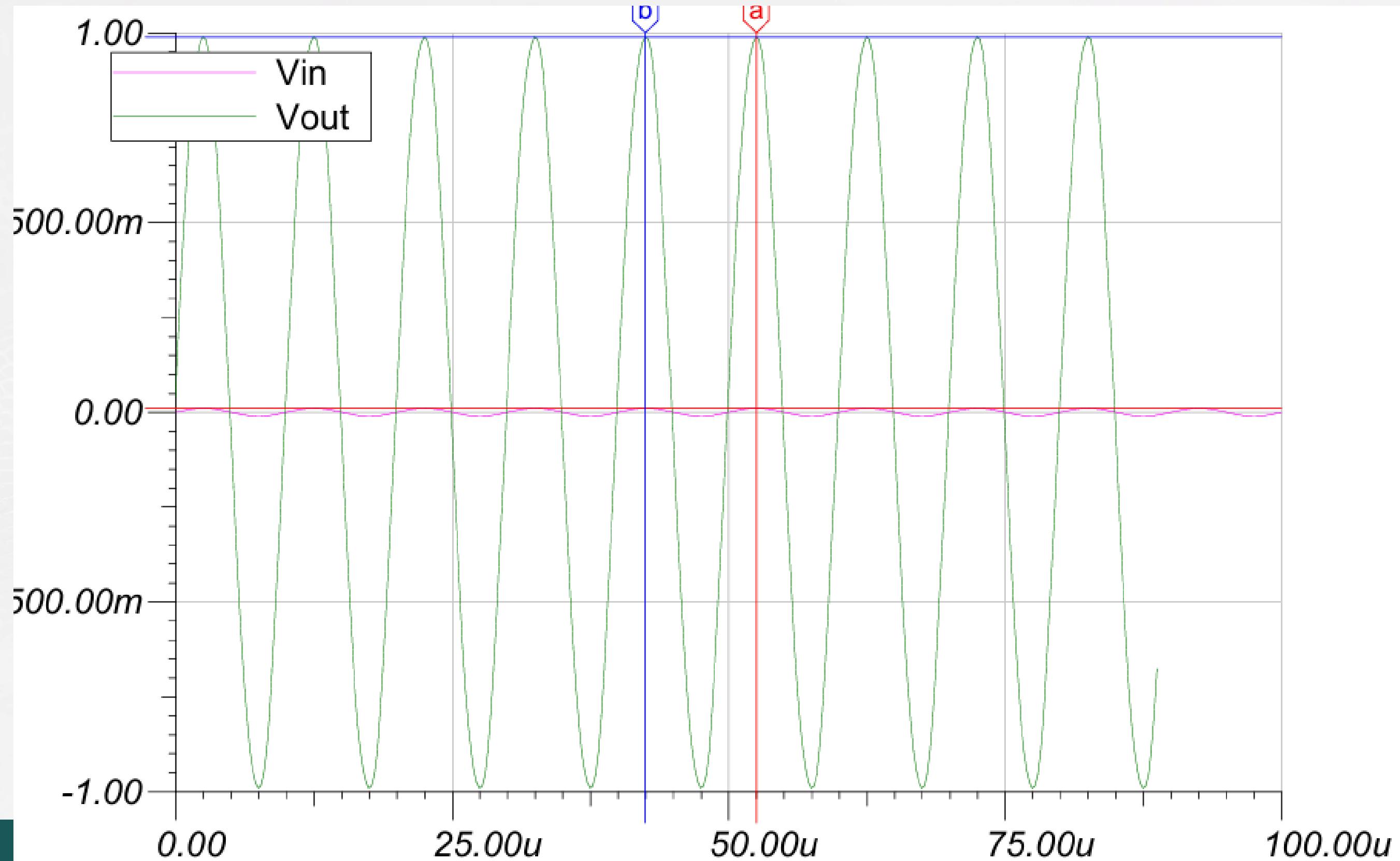


INA + CLIPPER FOR 50V INPUT

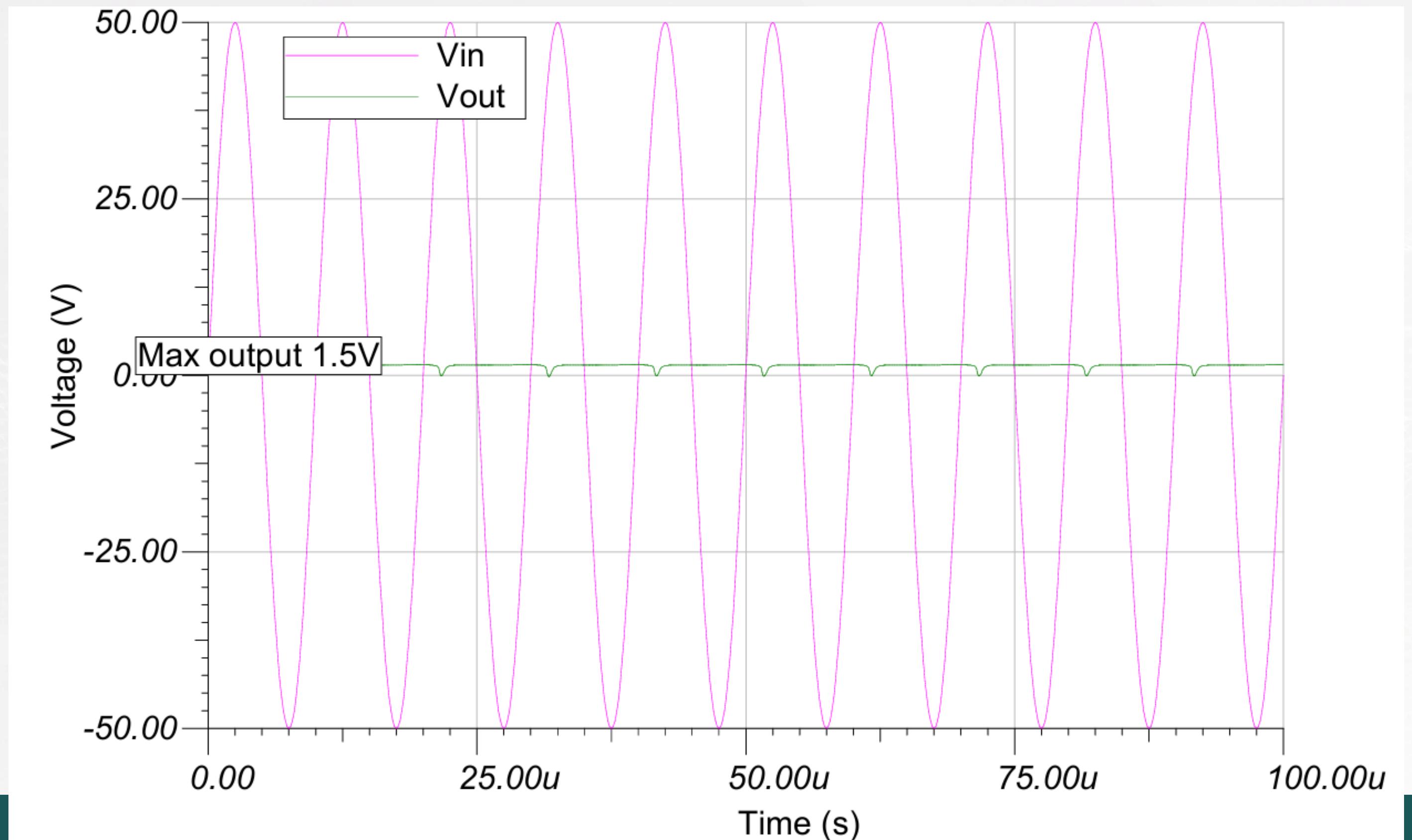


POWER AMPLIFIER

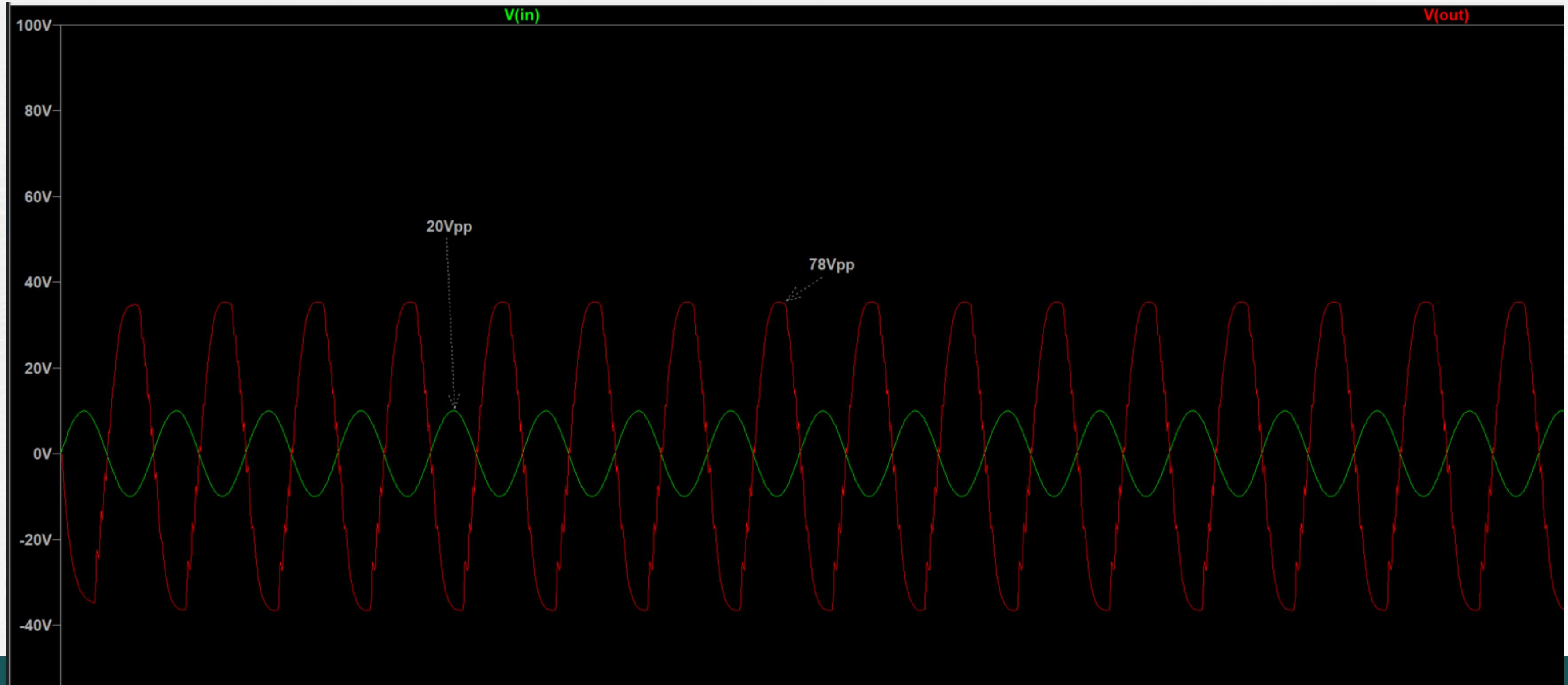


POWER AMPLIFIER

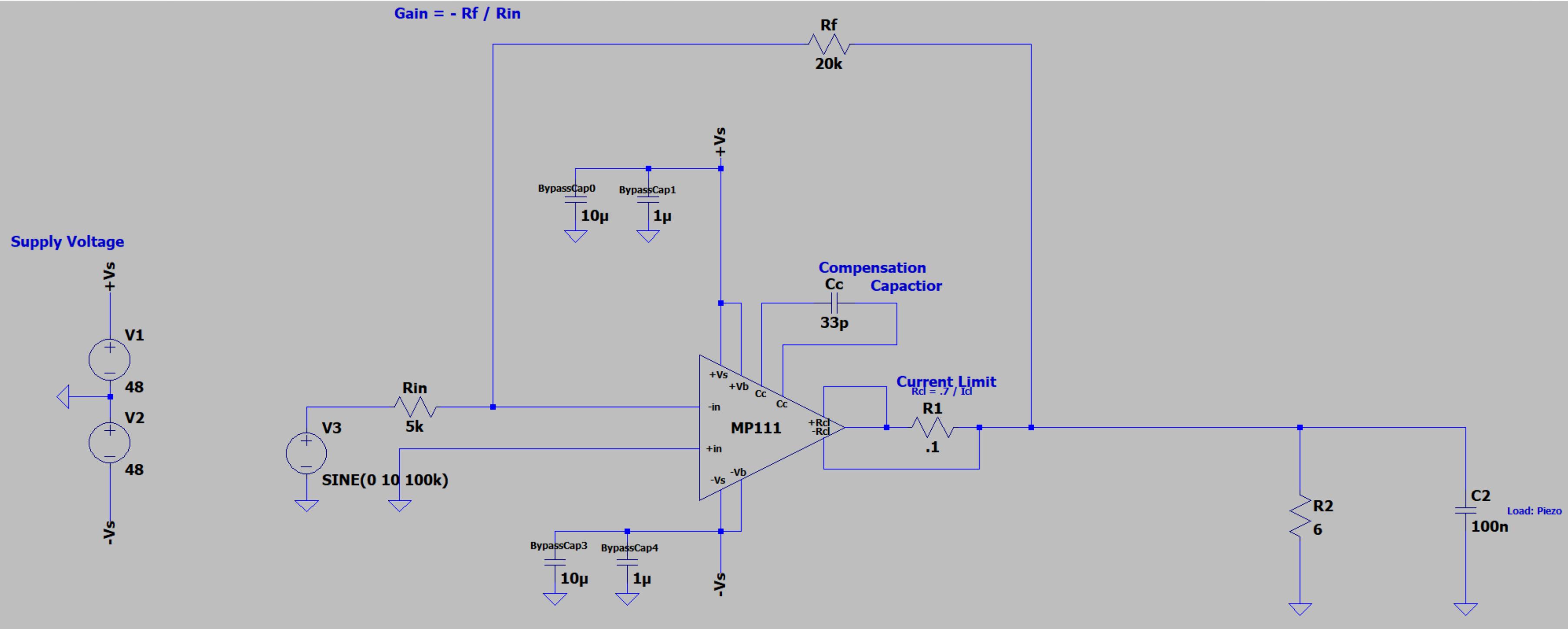

HANNING PULSE - PYTHON SIMULATION

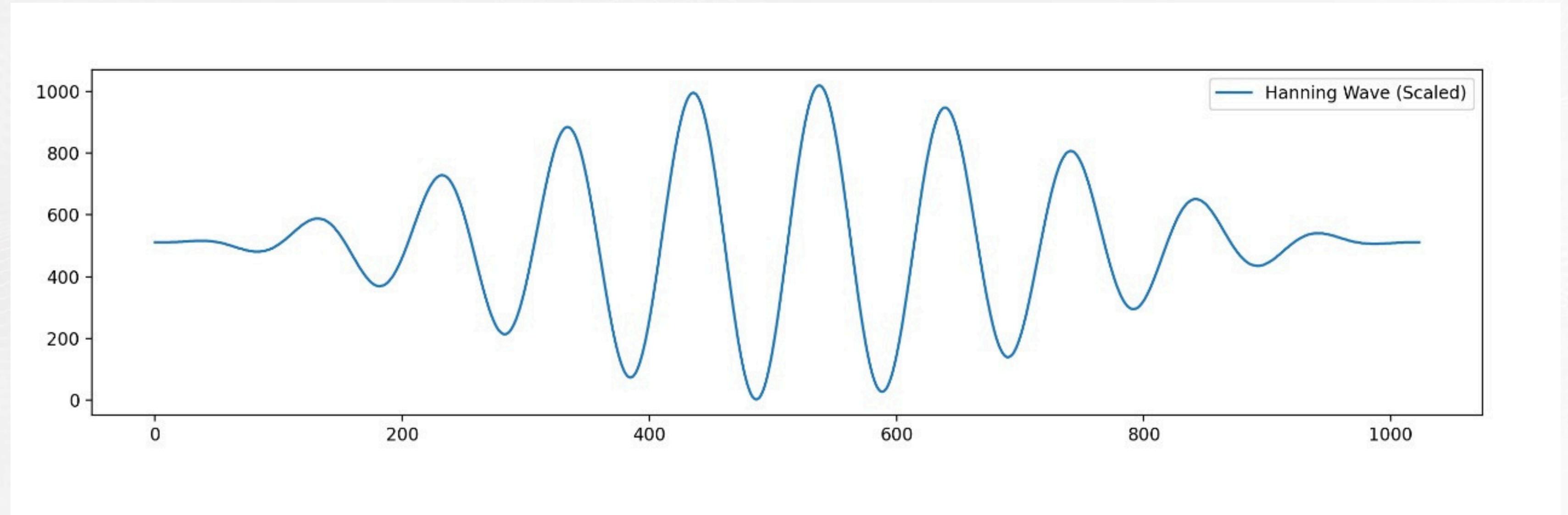

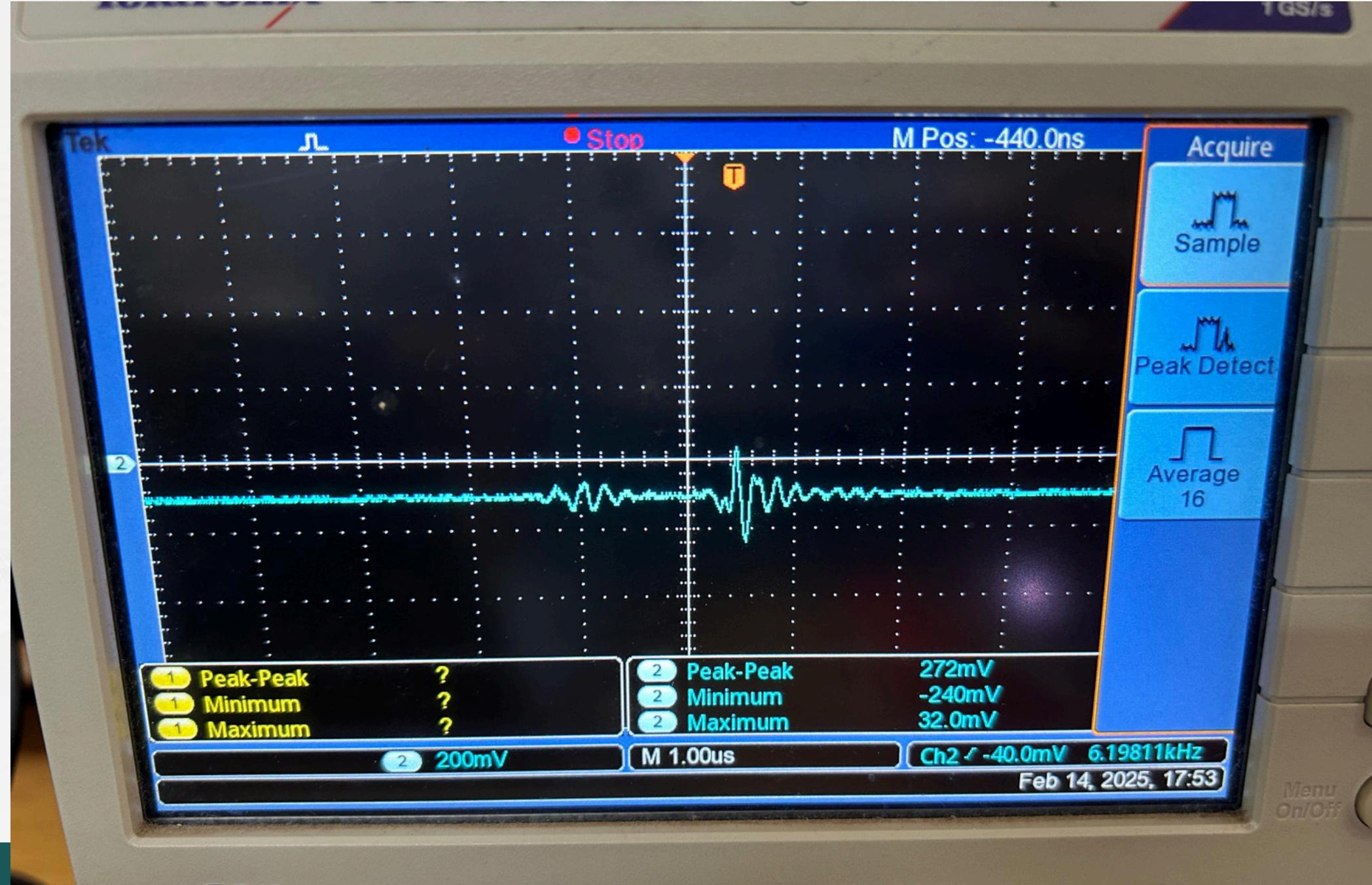HANNING PULSE ON DSO WITH LESSER SLEW RATE OPAMP (LM741)



COMSOL SIMULATIONS

Graphics

Function Plot X


Convergence Plot 1 X


▼

■



pw1(t) (V)

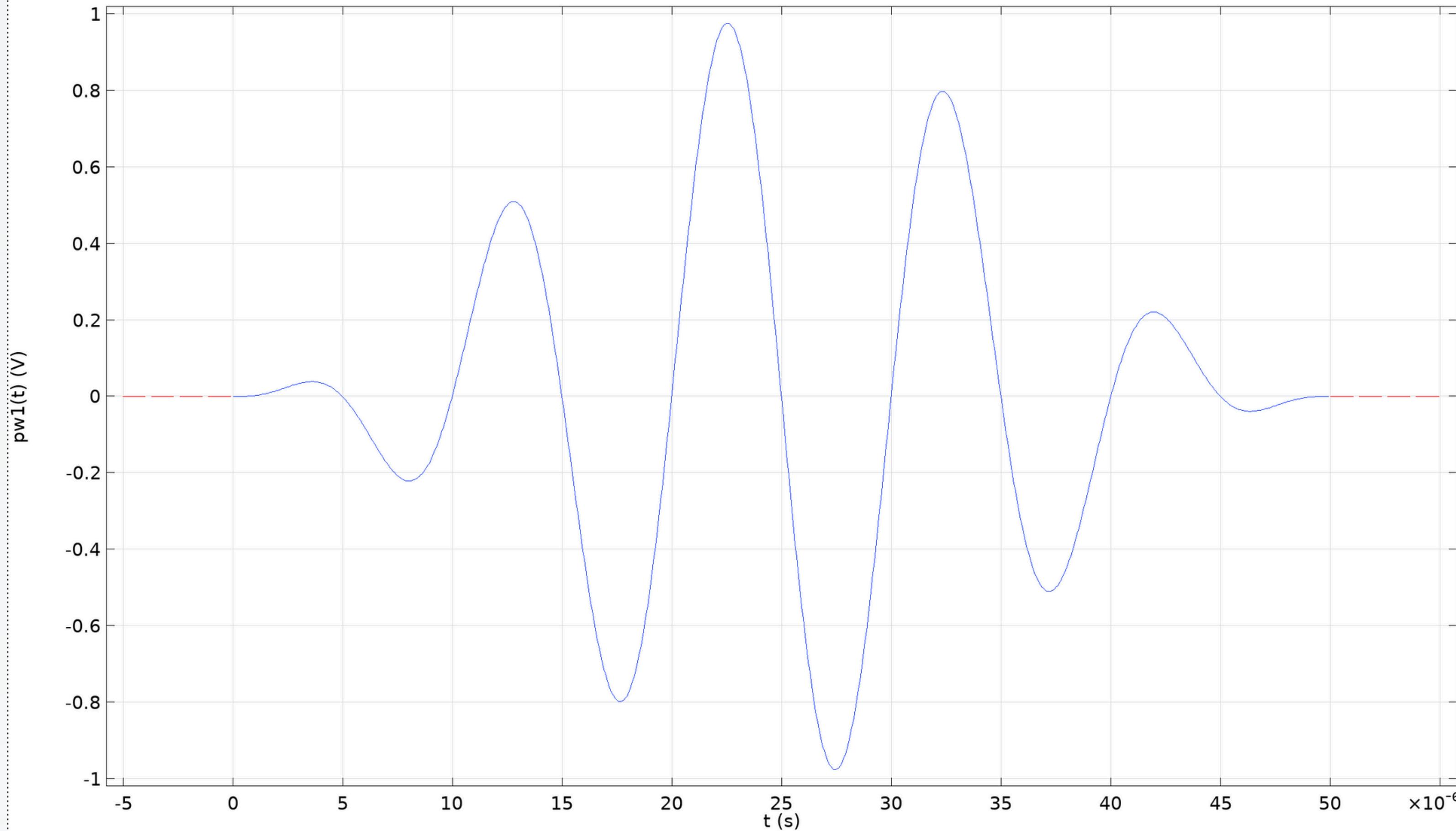


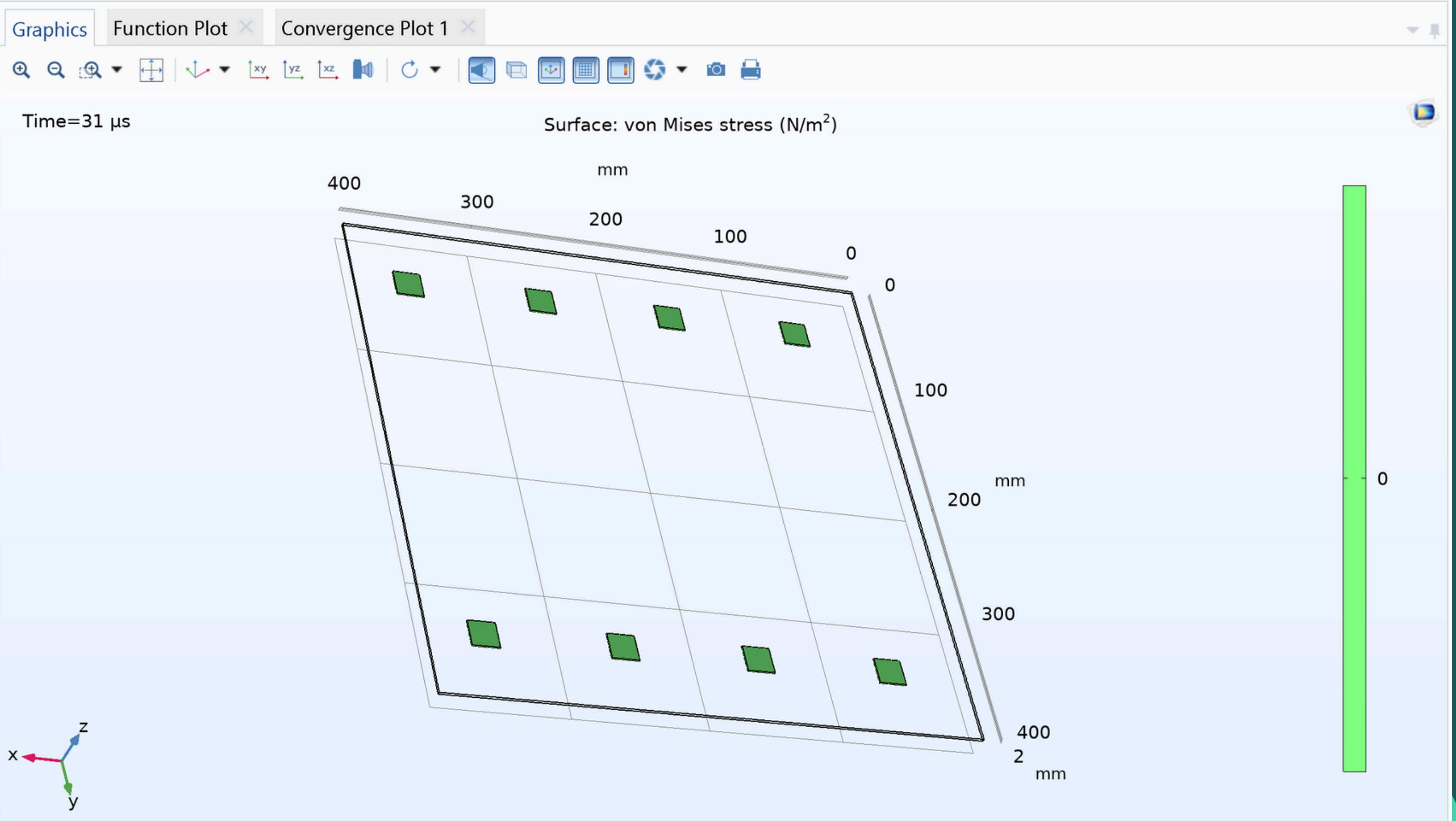

Messages Progress Log Evaluation 3D

0.85 e-12 AUTO 0.5 e-1 0.85 0.5 e-3 0.85 |

x	y	z	Value
261.87	343.55	3.0000	0.0000
256.66	349.28	3.0000	0.0000
163.18	348.23	3.0000	0.0000
56.215	344.78	3.0000	0.0000

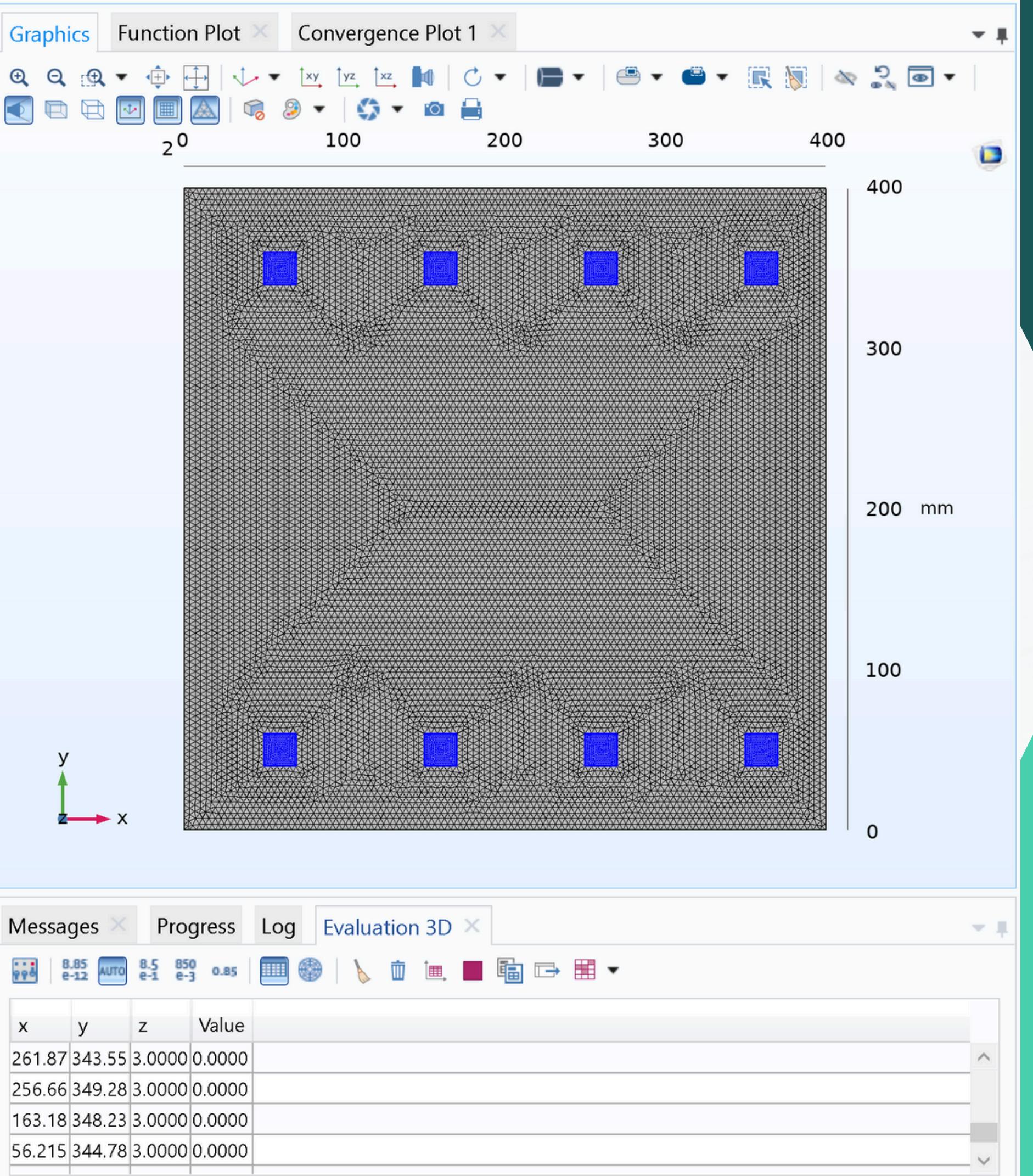


COMPLETE SCHEMATIC LINK



- https://drive.google.com/file/d/1pM-x1FfzuNWClZGZpETy26Dexs8zest_/view?usp=sharing

GANTT CHART FOR WORK DELEGATION

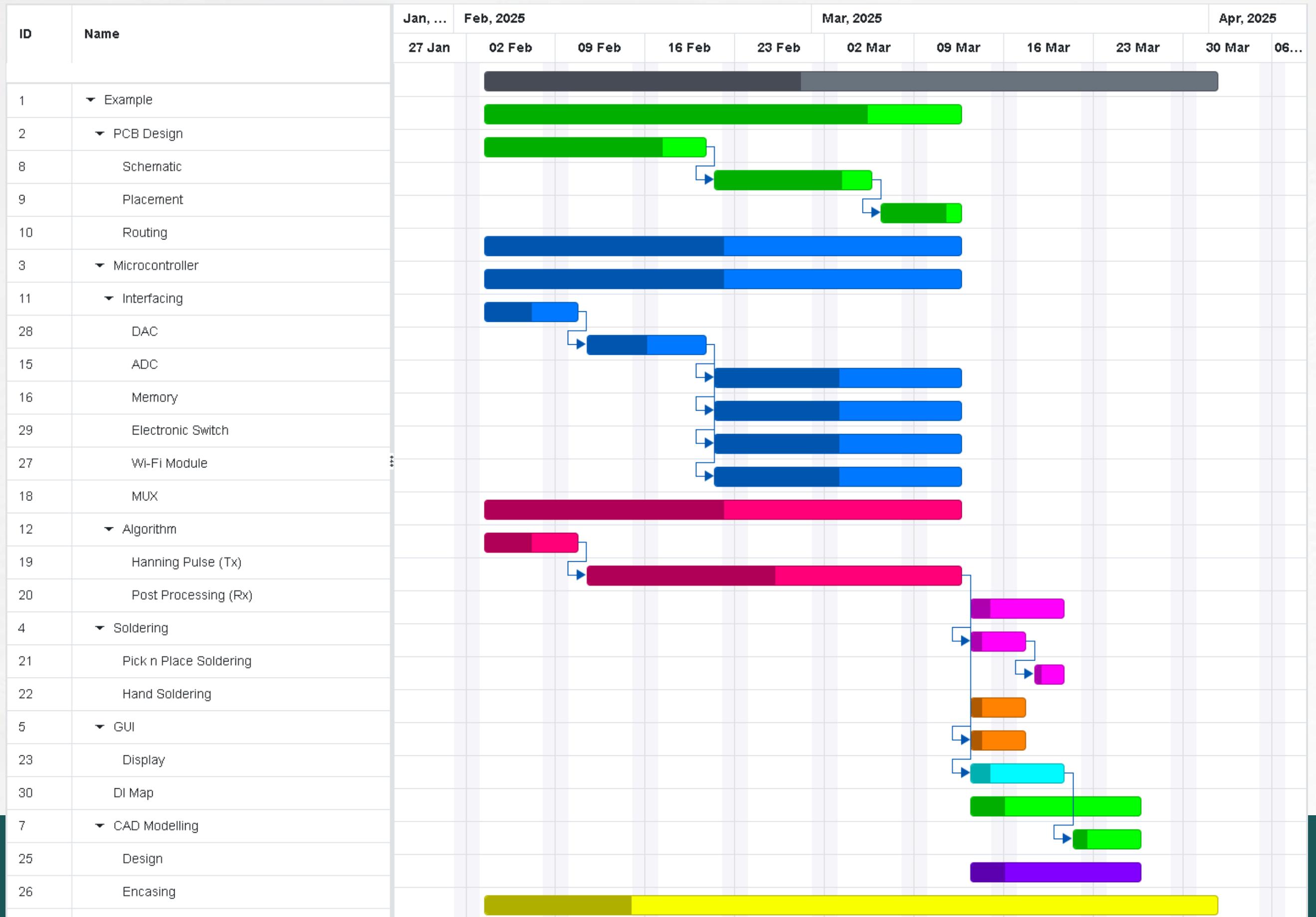


Deviations from original plan

- 1) We have now sub-divided our tasks into several more parts to be able to tackle various issues that may arise with each part efficiently.
- 2) Not all parts we needed to start PCB designing are available to us as a result we moved to algorithms and interfacing part and started it ahead while pushing soldering forward.
- 3) We spent some time on how to optimize providing power to various modules and reduced a few components by this method. This was because a few components had similar range of voltage requirements, so we decided to use fewer buck converters. This took us a few days.

DETAILS OF TEST PLANS

- **Preliminary testing**

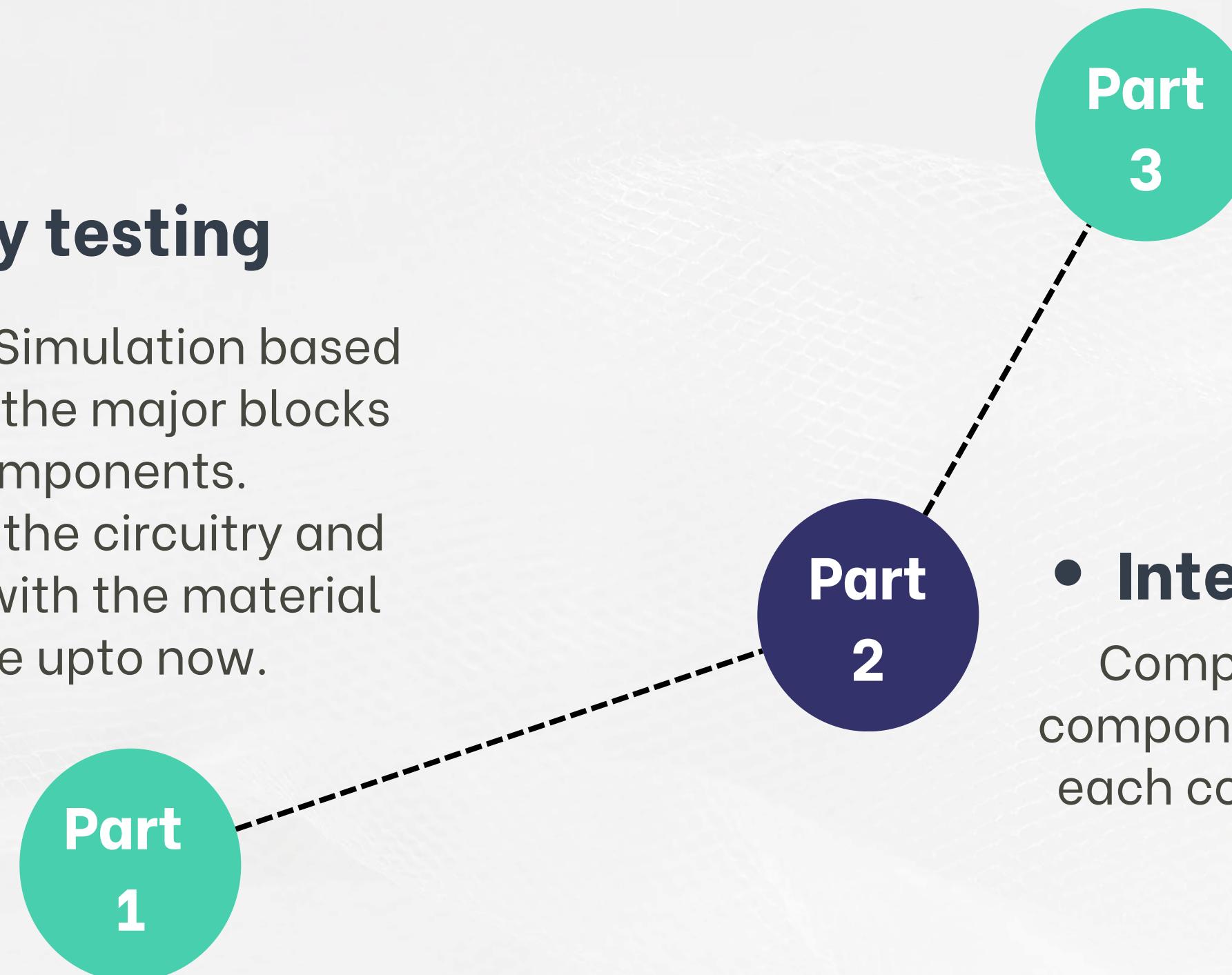1. Physical and Simulation based testing of all the major blocks and components.
2. Checking all the circuitry and connection with the material available upto now.



- **Final testing**

Running the complete handheld device with all the components onto an Al metal plate

- **Intermediate testing**

Complete testing once all the components are available once for each component and then taking blocks.

PRELIMINARY TESTING

- So we got a skewed Hanning pulse during our initial testing, this was due to the fact that we chose LM741 for our current-to-voltage converter, which has a lower slew rate. So the high transitions per sample weren't generated well.
- So we now have chosen TL072 which has a higher slew rate.
- This will ensure we sample the values and subsequently create the right analog waveform.
- Power Amplifier: Worked correctly on simulations and will next test on breadboard.



Thinking ahead to next milestone

- Upon receiving all the components we will finish the individual component simulations and physical testing by making the required circuitry .
- Then we will move onto writing the required code on uC and check for the proper functioning of the circuitry after dumping the code.
- After that we will let the PCB design (including the power amplifier) reviewed and once finalized take it to fabrication.
- Then we will test onto the PCB and CAD combined model and do the subsequent debugging.
- Once all that is finalized we will work on making a working prototype which will be a handheld device.